

Integer Multiplication

Multiplying two numbers:

multiplicand		1	0	1	0		
multiplier	×	1	0	0	1		
			1	0	1	0	
		0	0	0	0		
	0	0	0	0			
+	1	0	1	0			
		1	0	1	1	0	1
							0


$m\text{-bits} \times n\text{-bits} = (m + n)\text{-bit result}$

$m\text{-bits}$: $2^m - 1$ is the largest number

$$\Rightarrow (2^m - 1)(2^n - 1) = 2^{m+n} - 2^m - 2^n + 1$$



Integer Multiplication: First Try

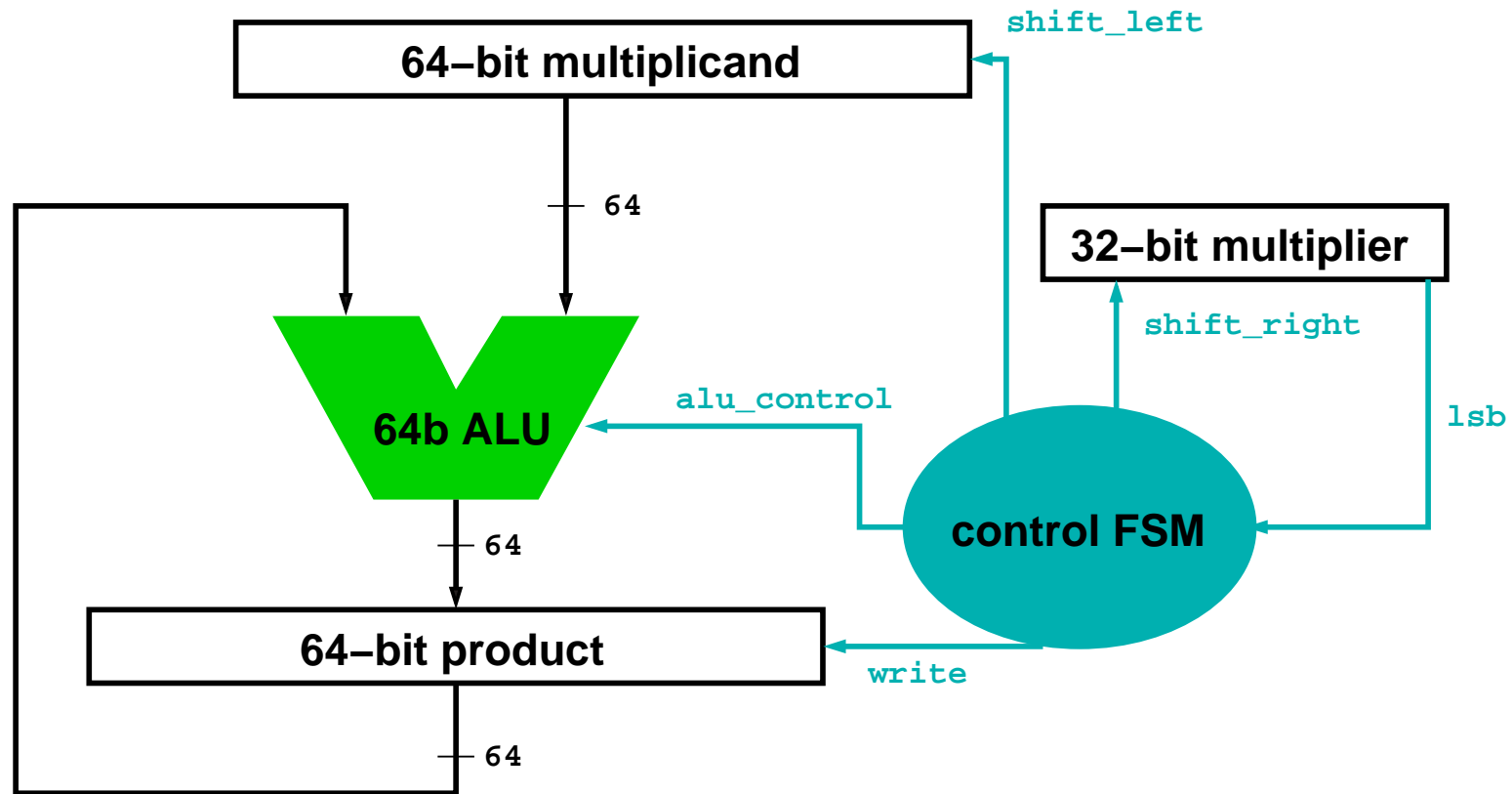


How do we build this?




Registers And Shift Registers


Register with shift left:

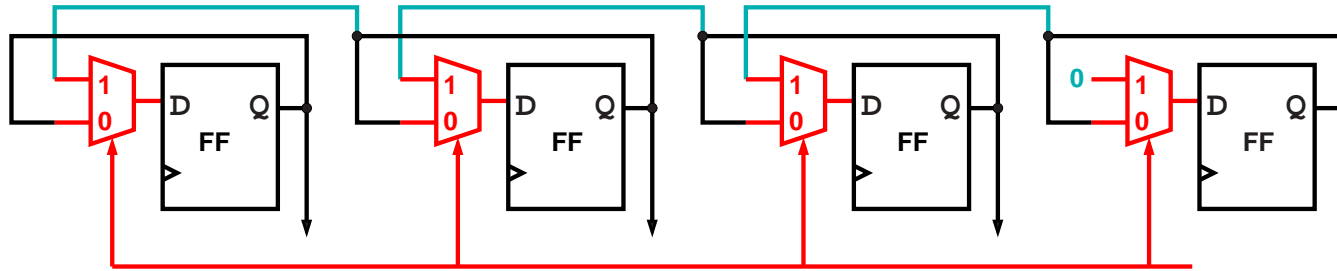

Register with write:

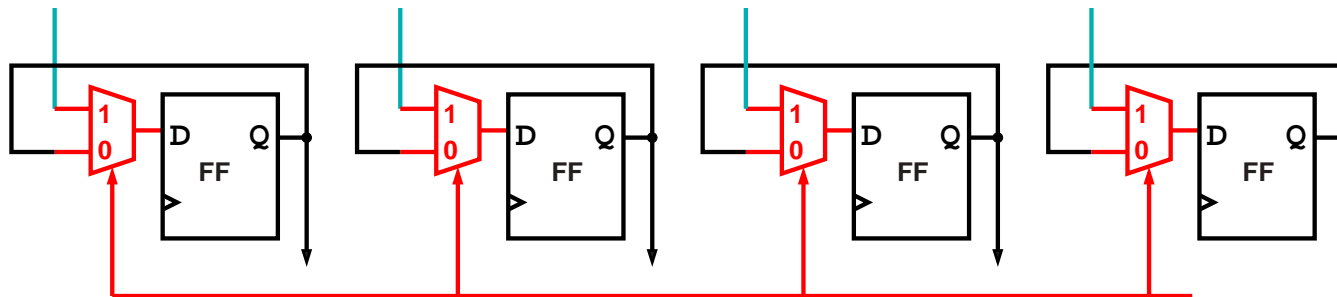

Control

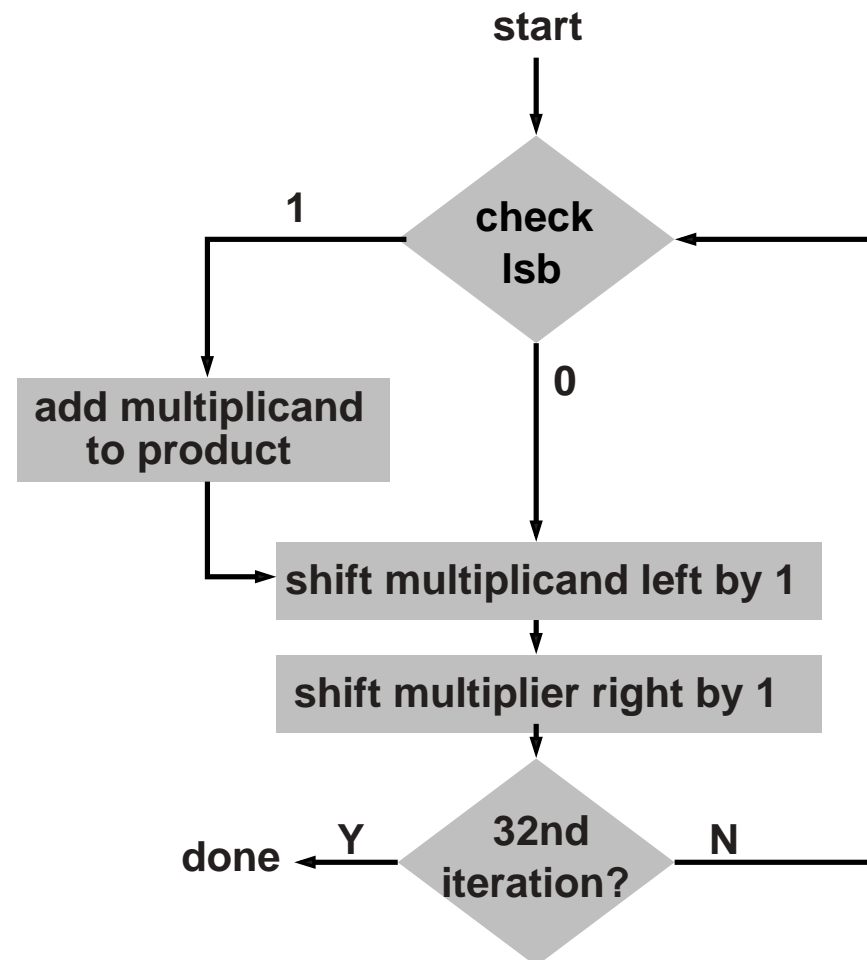


Integer Multiplication

Observations:


- 32 iterations for multiplication \Rightarrow 32 cycles
- How long does 1 iteration take?
- Suppose 5% of ALU operations are multiply ops, and other ALU operations take 1 cycle.
 $\Rightarrow CPI_{alu} = 0.05 \times 32 + 0.95 \times 1 = 2.55!$
- Half of the bits of the multiplicand are zero
 \Rightarrow 64-bit adder is wasted
- 0's inserted when multiplicand shifted left
 \Rightarrow product LSBs don't change



Using A 32-Bit ALU

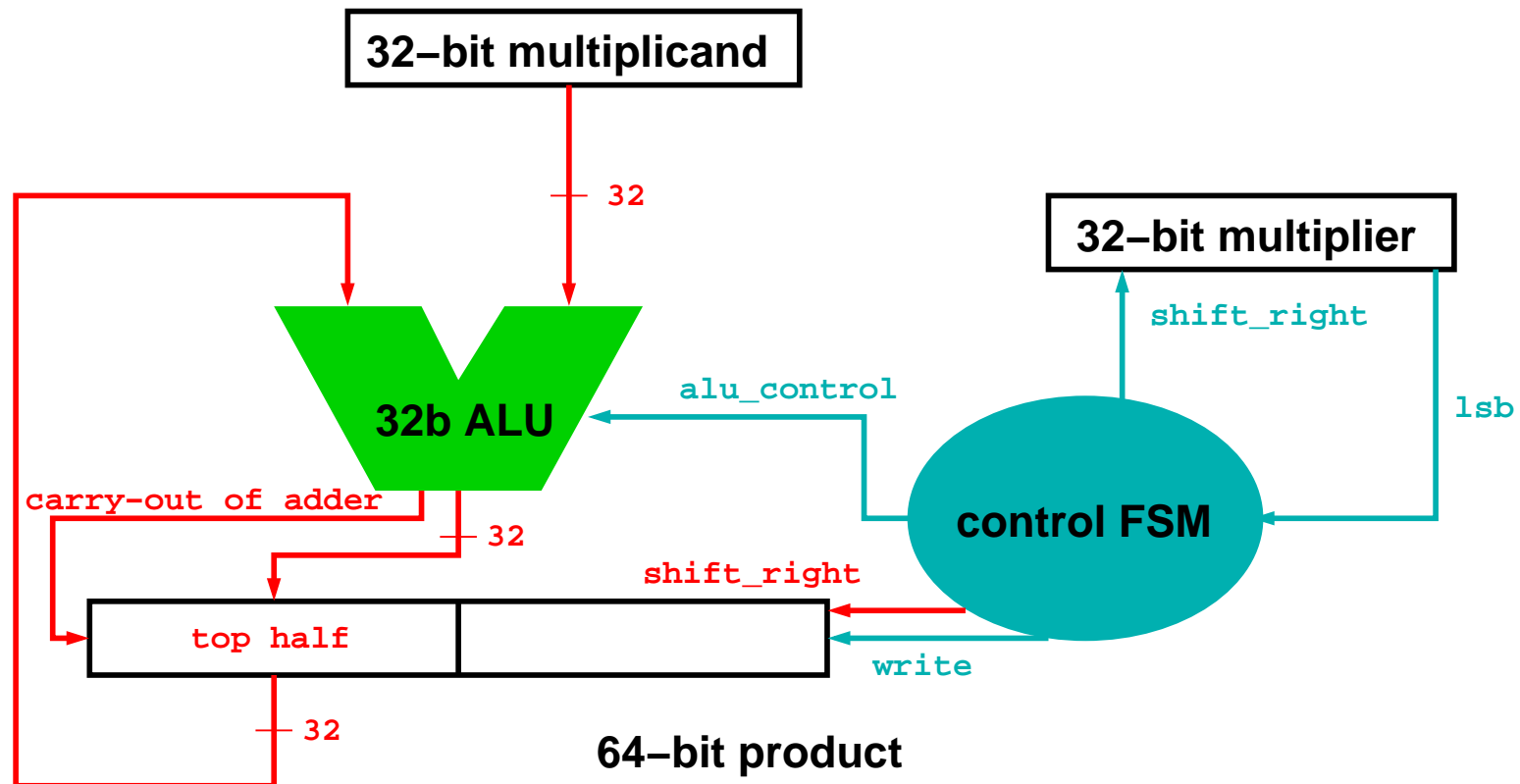

New Control

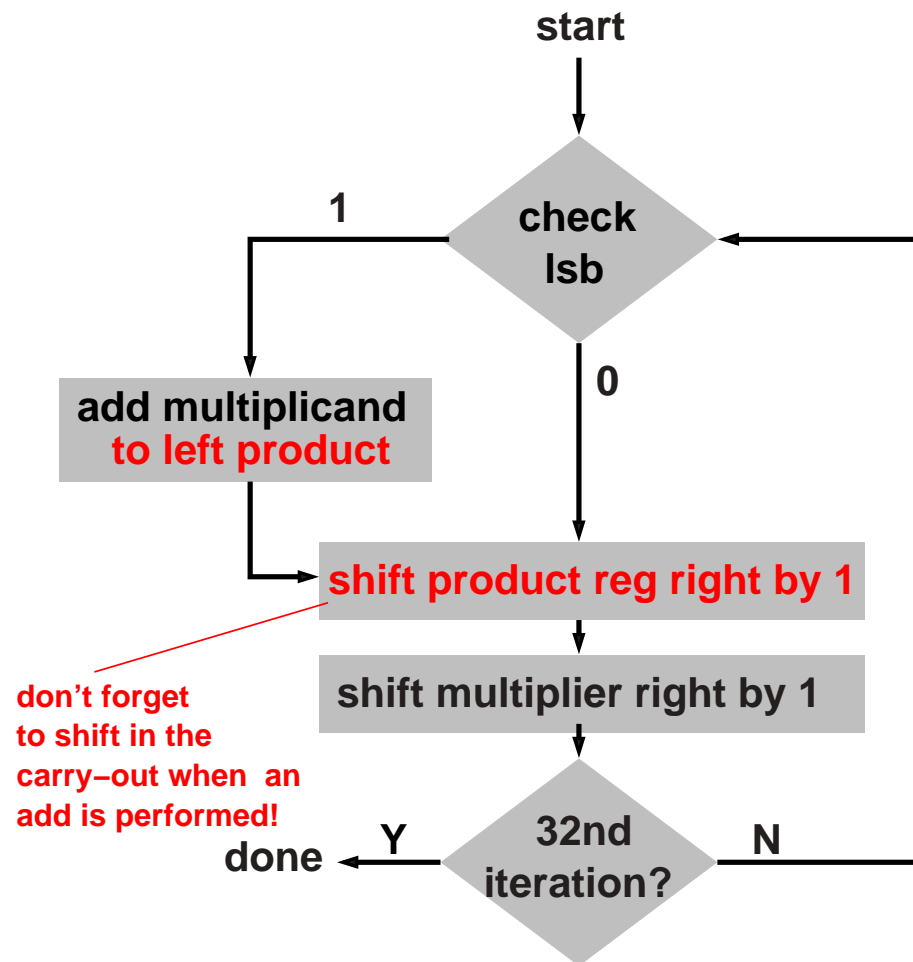


Bottom half of product register is zero initially.

Each iteration:
adds 1 product bit
loses one multiplier bit


Share storage for product register and multiplier!




Integer Multiplication Hardware

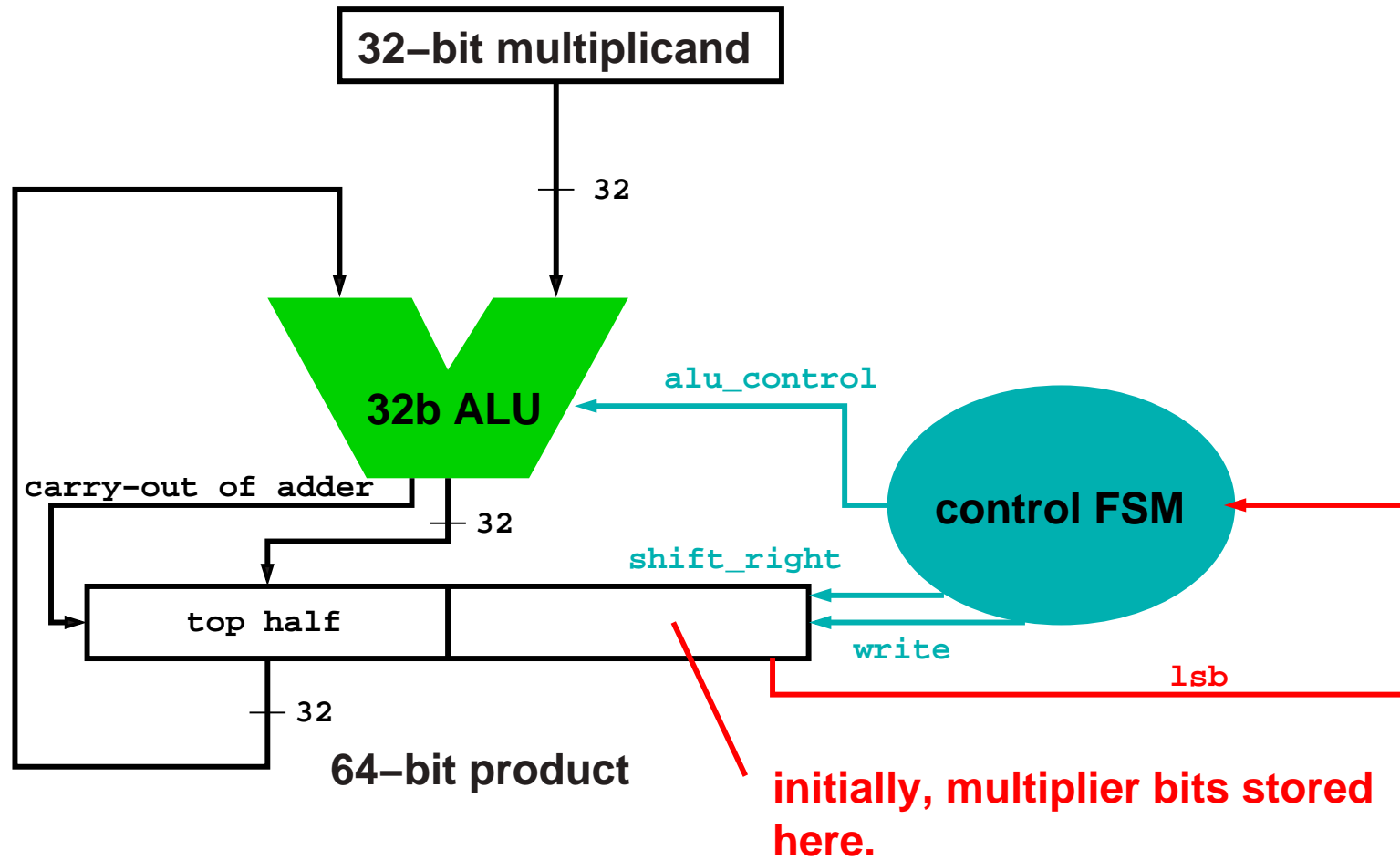


Integer Multiplication Hardware

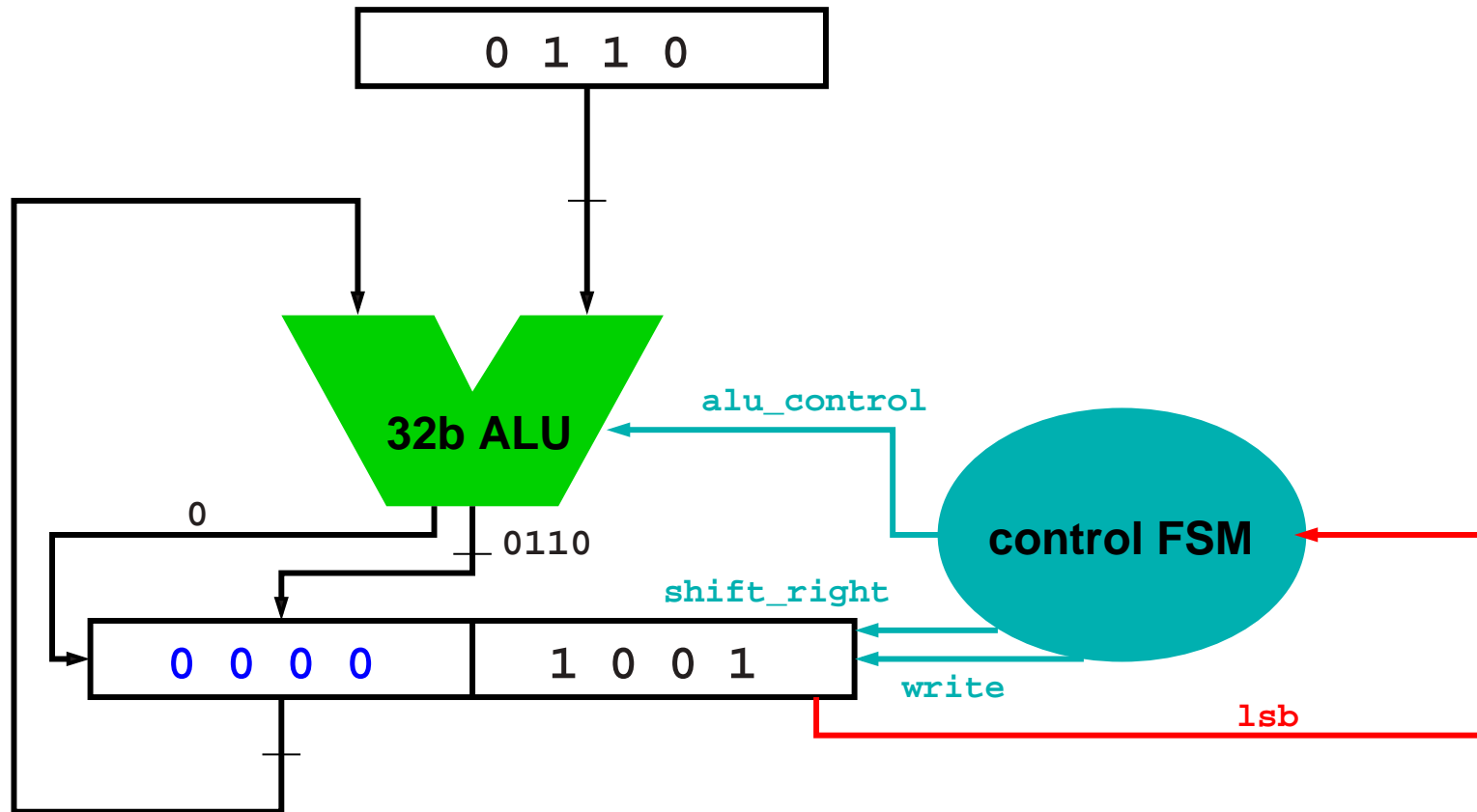


Integer Multiplication Hardware

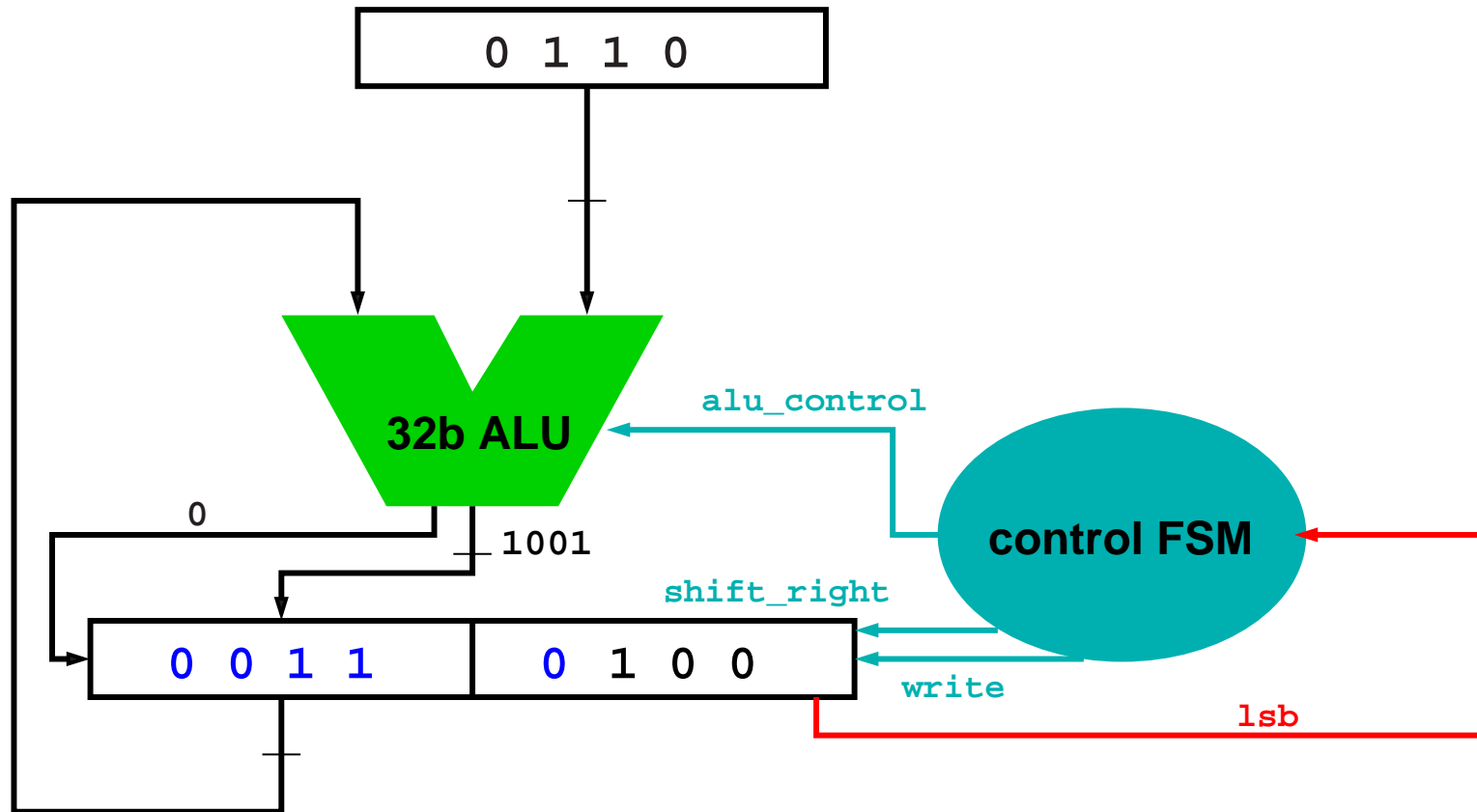


Integer Multiplication Hardware

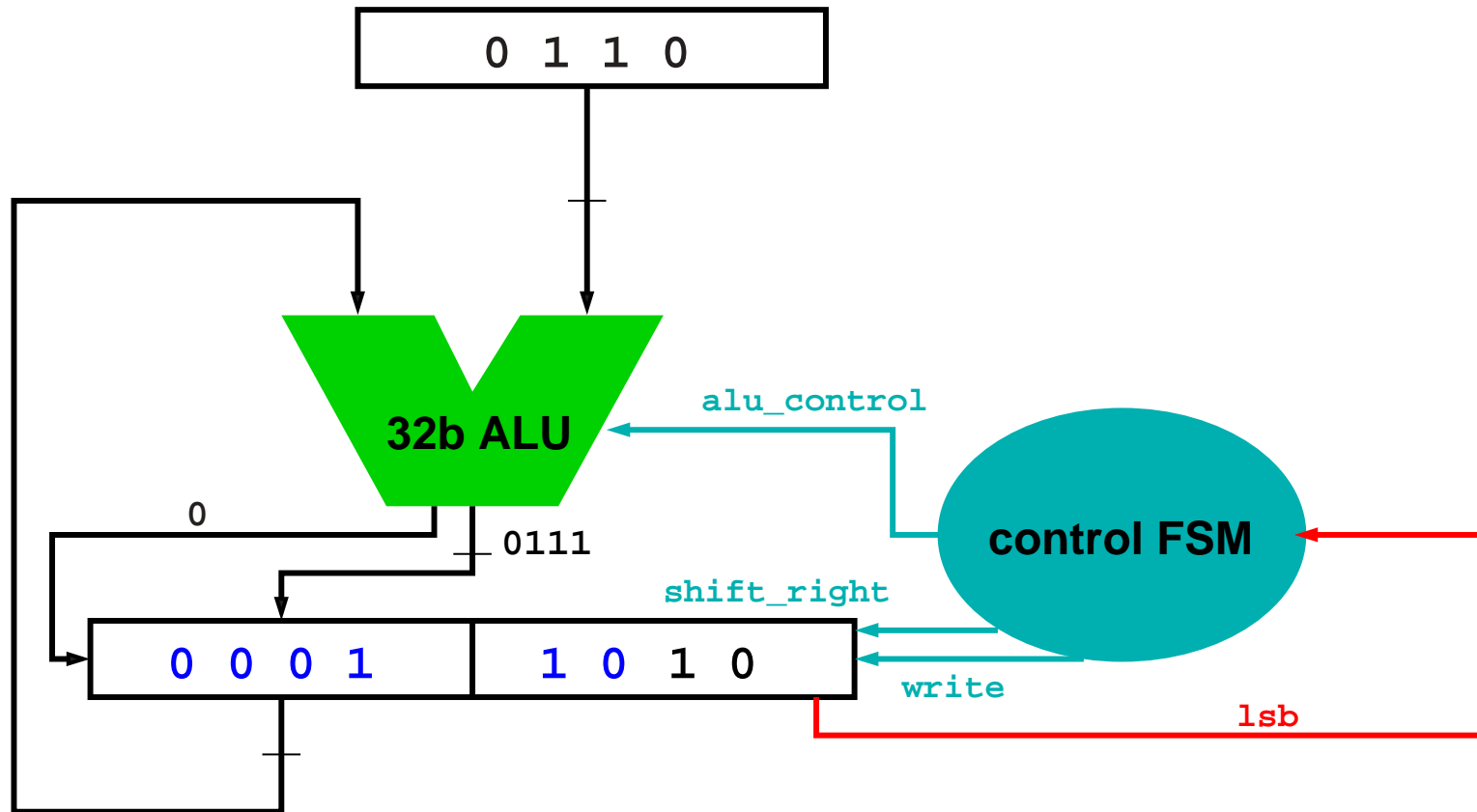

Integer Multiplication Hardware

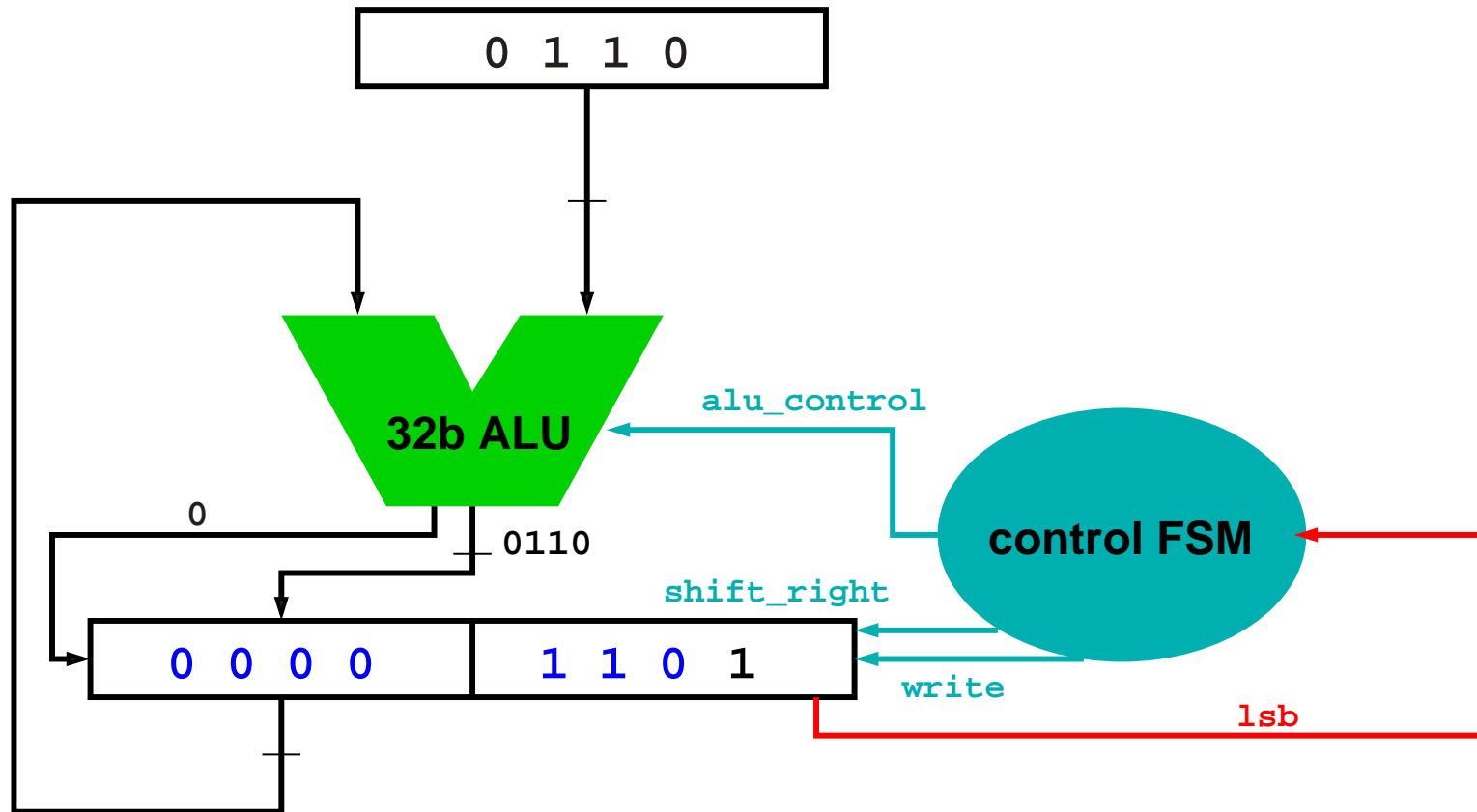

Integer Multiplication Hardware

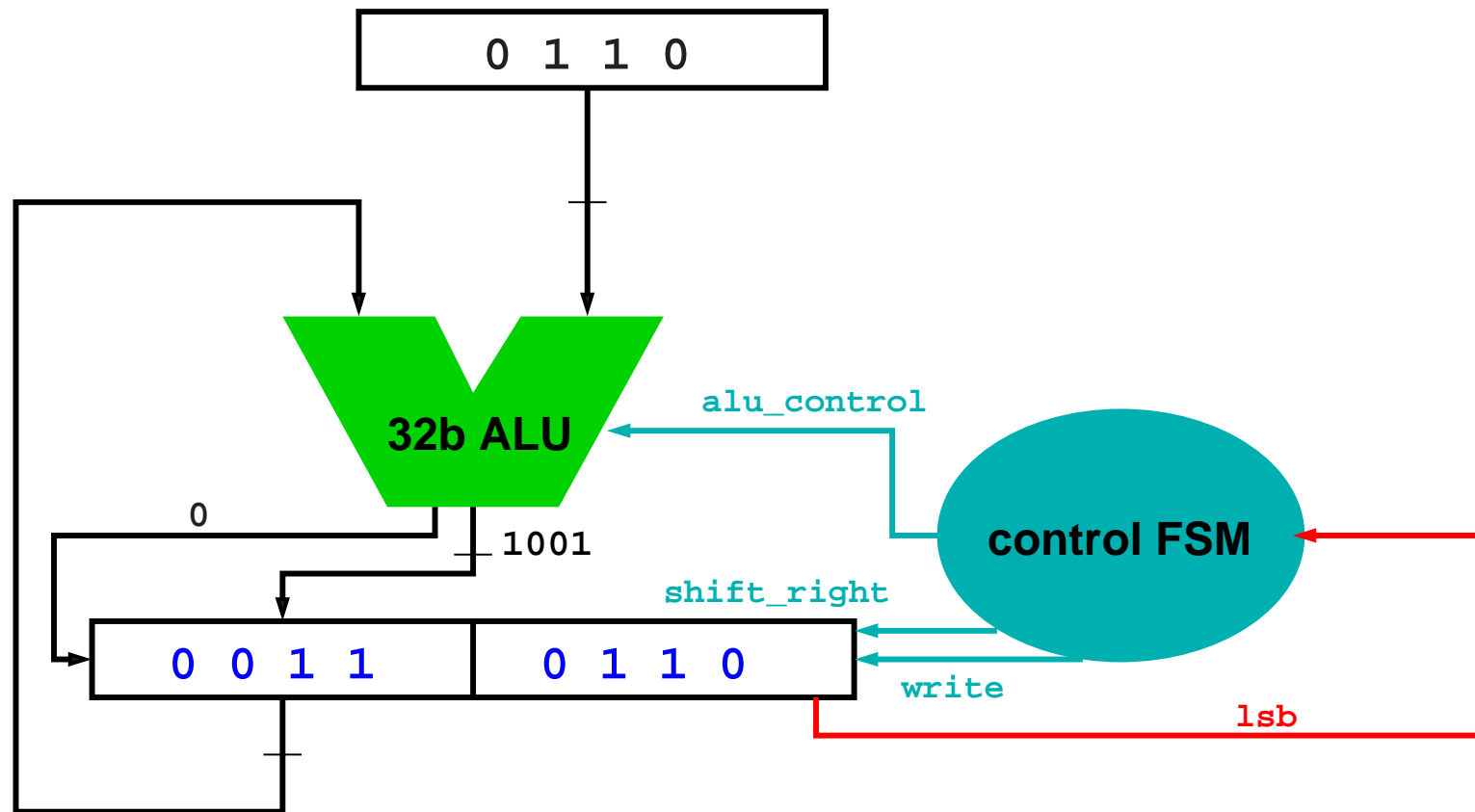

Integer Multiplication

- Each step requires an add and shift
- MIPS: `hi` and `lo` registers correspond to the two parts of the product register
- Hardware implements `multu`
- Signed multiplication:
 - Determine sign of the inputs, make inputs positive
 - Use `multu` hardware, fix up sign
 - Better: Booth's algorithm



Booth Multiplication

Example:

multiplicand							
multiplier	×	1	0	1	0		
		0	1	1	0		
			0	0	0	0	
			1	0	1	0	
			1	0	1	0	
+		0	0	0	0		
		0	1	1	1	1	0
		0	1	1	1	0	0


Instead we could subtract early and add later...

$$6x = 2x + 4x = -2x + 8x$$

$$11110000 = 10000XXXX - 0001XXXX$$



Booth Multiplication

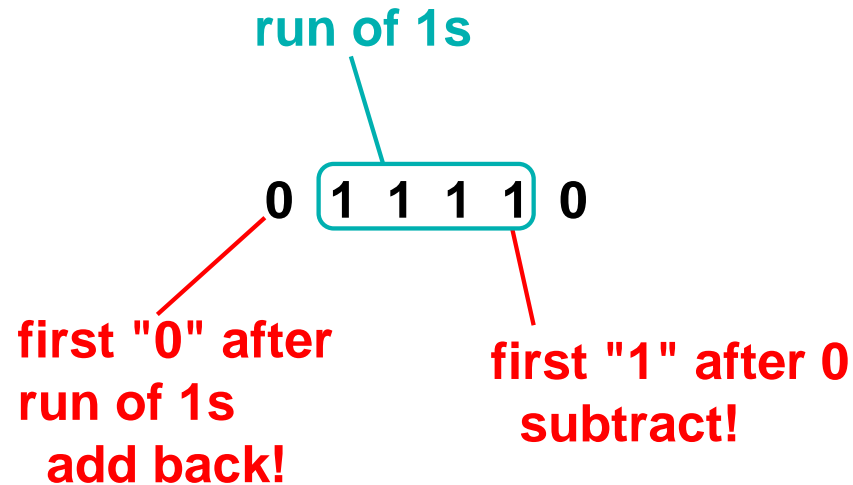

Current	Right	Explanation
1	0	beginning of run of 1s
0	1	end of run of 1s
1	1	middle of run of 1s
0	0	middle of run of 0s

Originally for speed: shifts faster than adds



Booth Multiplication

Depending on current and previous bits, do one of the following:

- 00: middle of a run of 0s \Rightarrow no operation
- 01: end of a run of 1s \Rightarrow add multiplicand to left half of product
- 10: start of a run of 1s \Rightarrow subtract multiplicand from left half of product
- 11: middle of a run of 1s \Rightarrow no operation

As before, shift product register right by 1 bit per step.



Integer Division

		0101	quotient
divisor	0010	$\overline{)1011}$	dividend
		0010	
		- 0010	
		\hline 0011	
		0010	
		- 0010	
		\hline 0001	remainder

Red: steps where subtracting would result in a negative number, i.e. quotient bit is zero.




Integer Division

		0101	quotient
<i>divisor</i>	0010	1011	<i>dividend</i>
		00010000	
	-	00001000	
		00000011	
		00000100	
	-	00000010	
		00000001	<i>remainder</i>


Pad out the dividend and divisor to 8 bits.



Integer Division

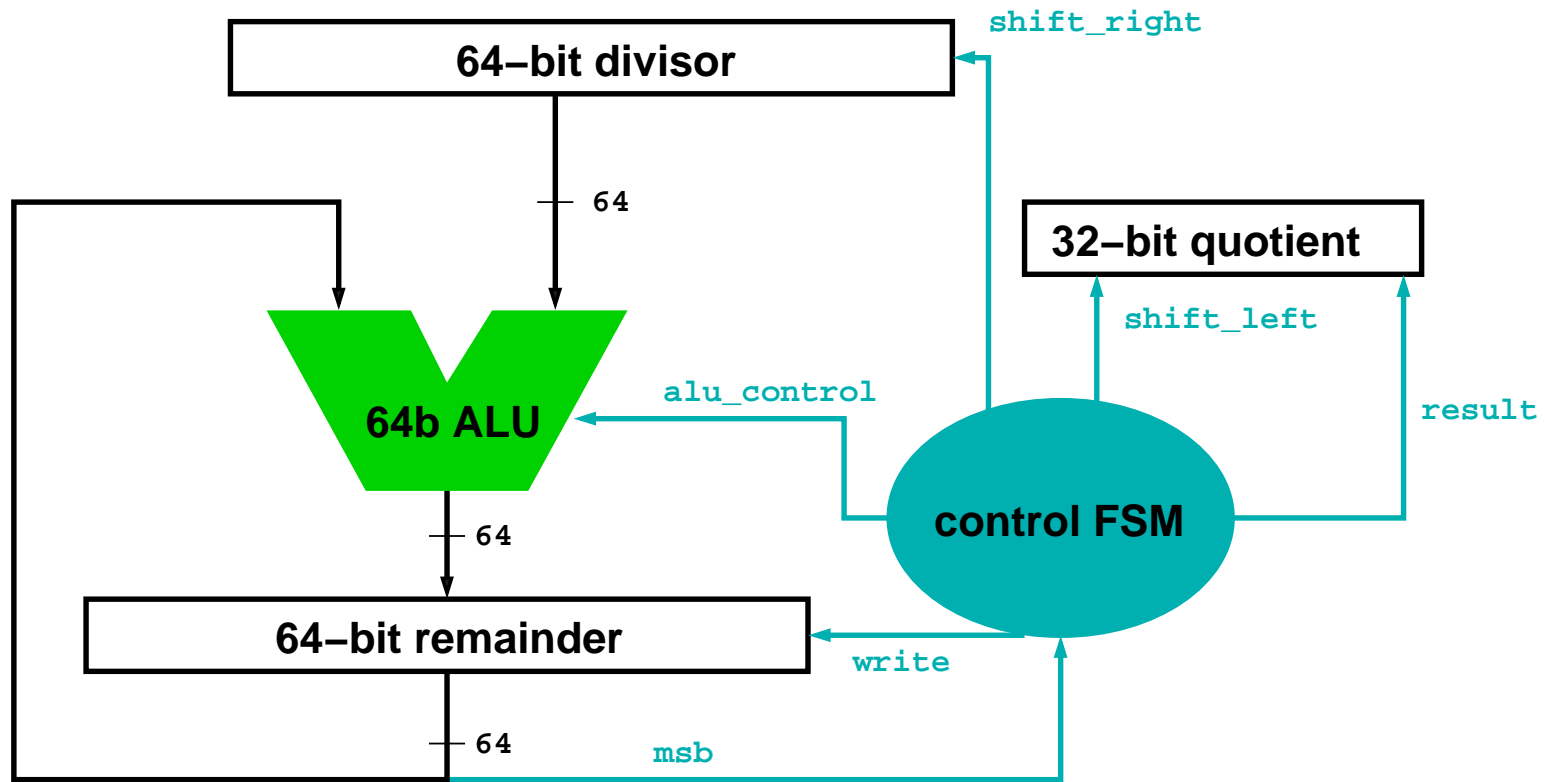

Integer Division

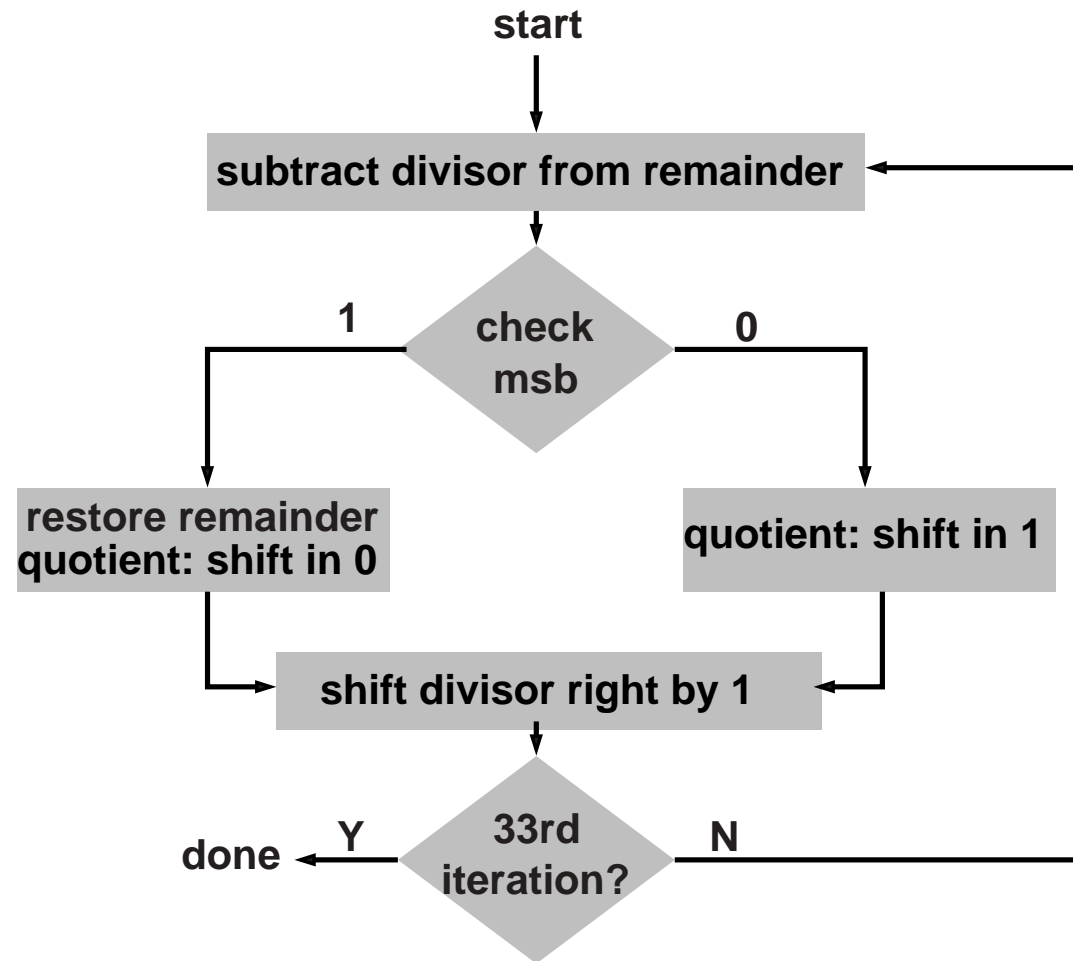

Integer Division


Observations:

- Half the bits in the divisor are zero
⇒ 64-bit ALU wasted
- Instead of shifting divisor right, we can shift remainder left
- When does the first iteration shift in a 1 into the quotient?
⇒ save 1 iteration


What is the initial value of the divisor?



Integer Division

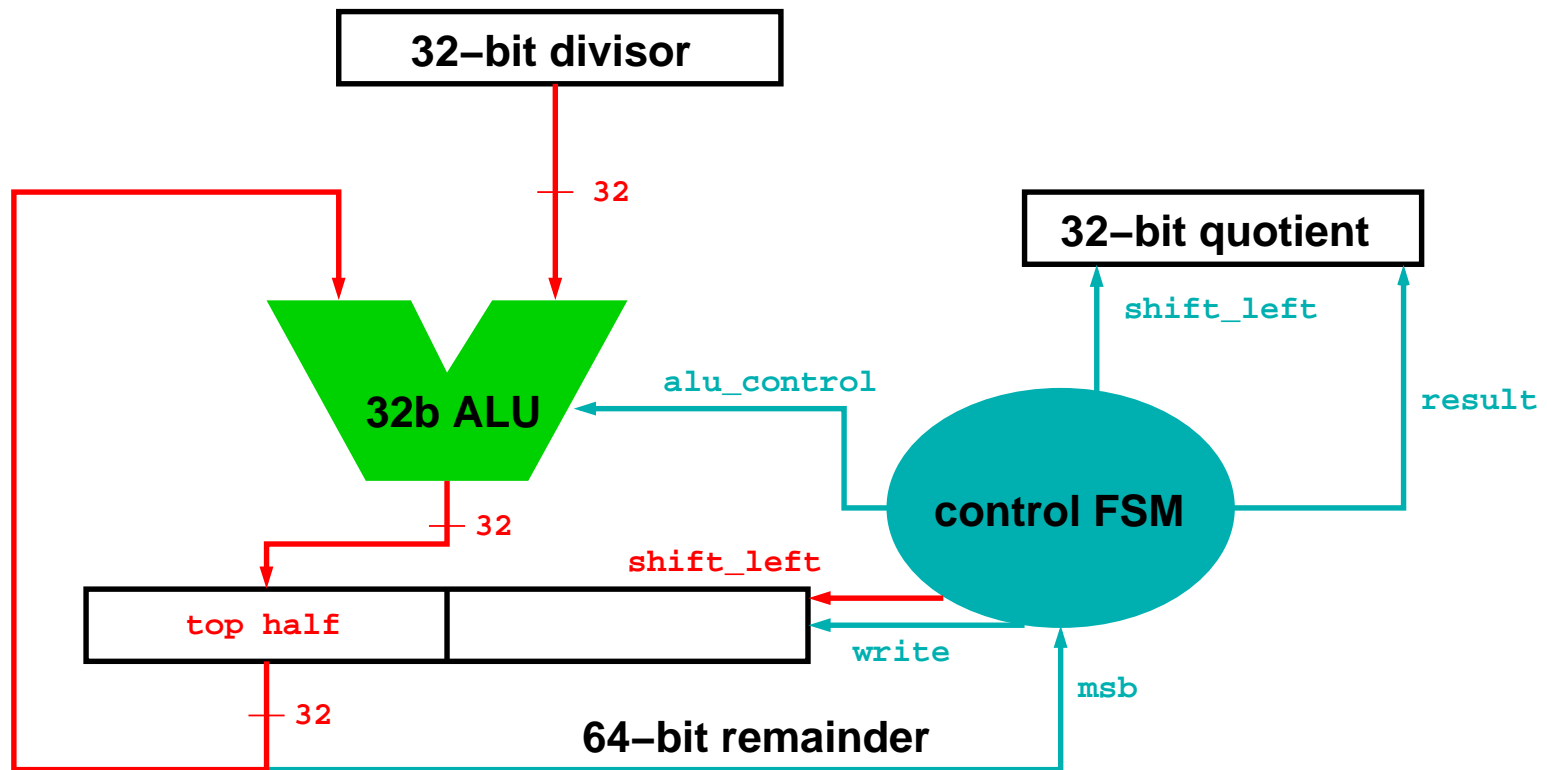

New Control

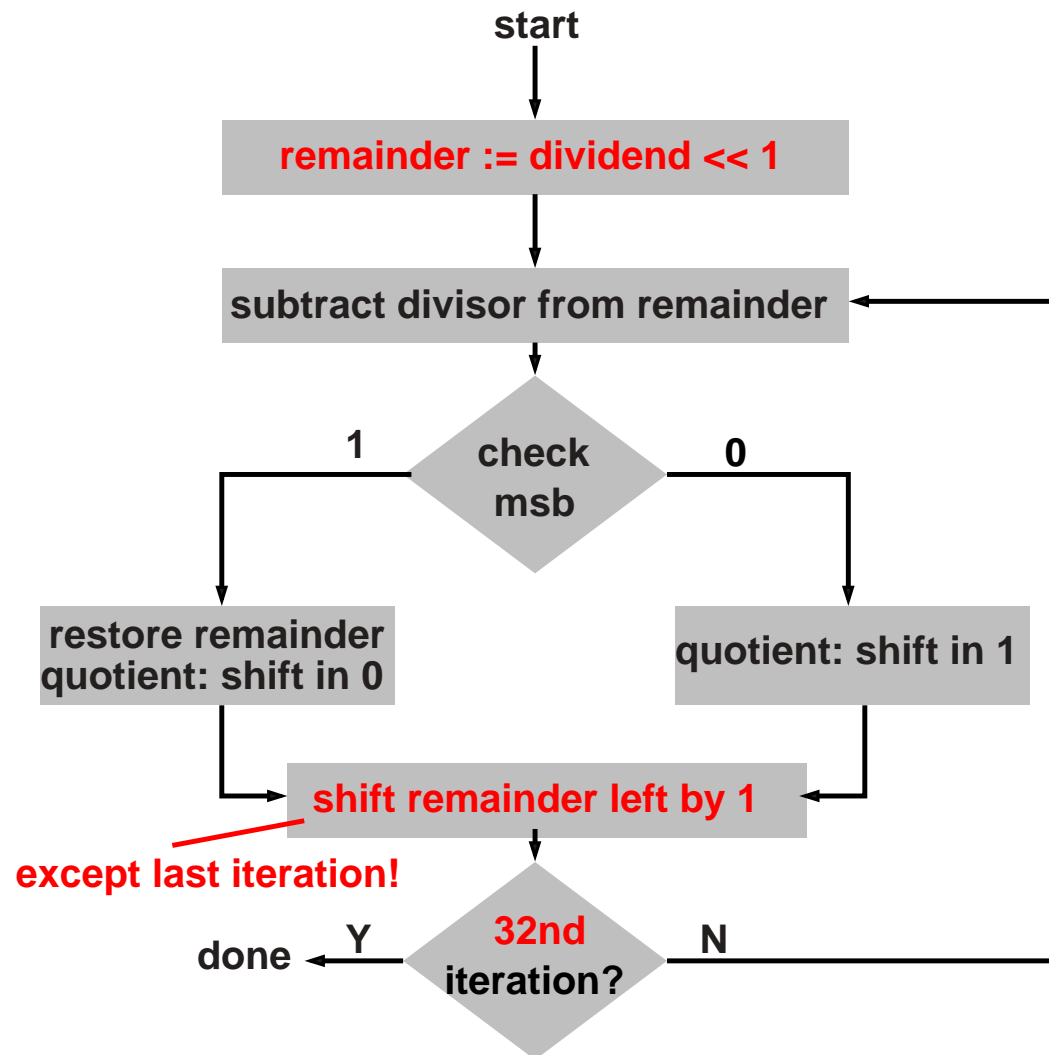


Remainder loses one bit per iteration;

Quotient gains one bit per iteration.


=> share registers!



Final Divider Hardware

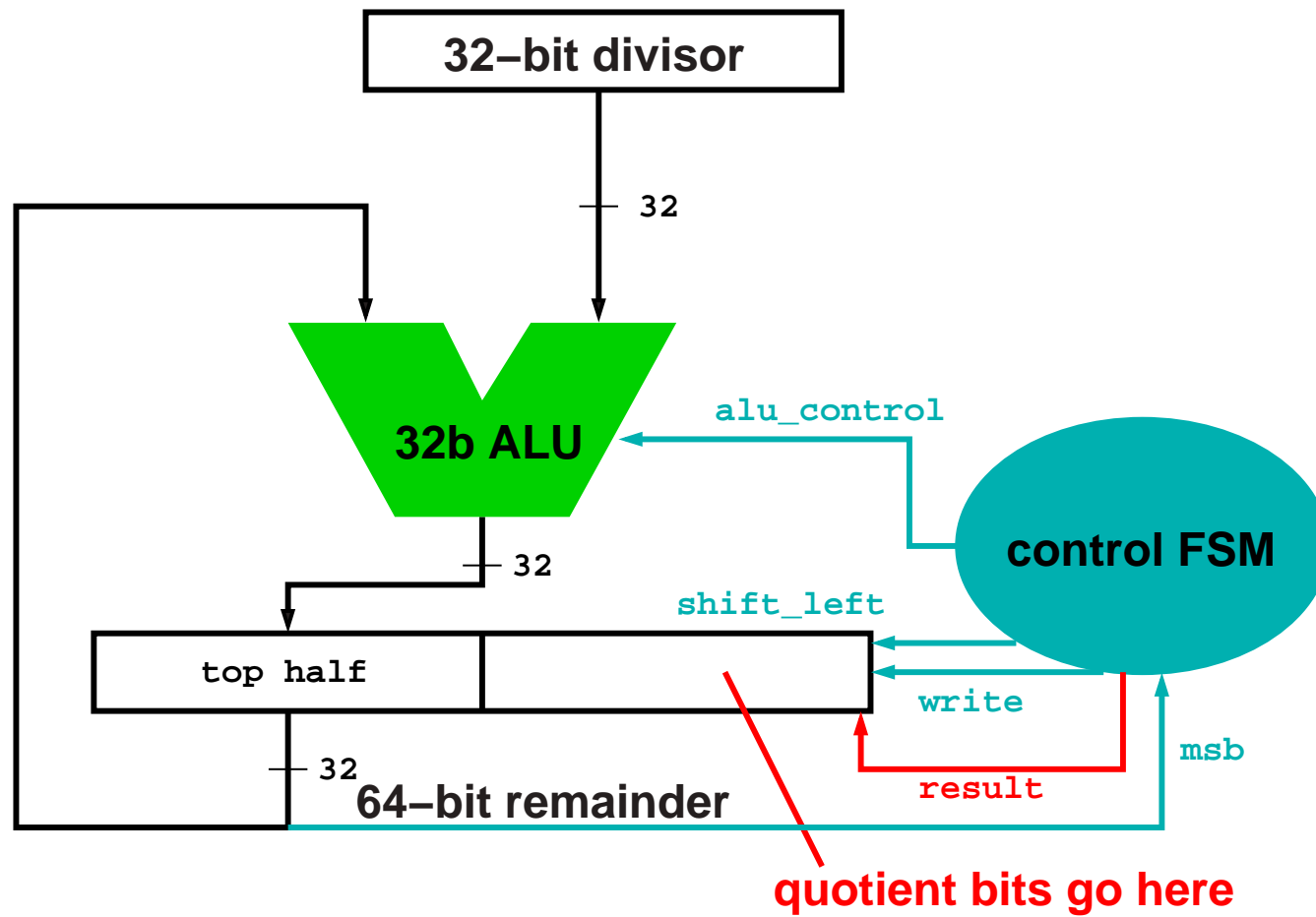

Mult/Div

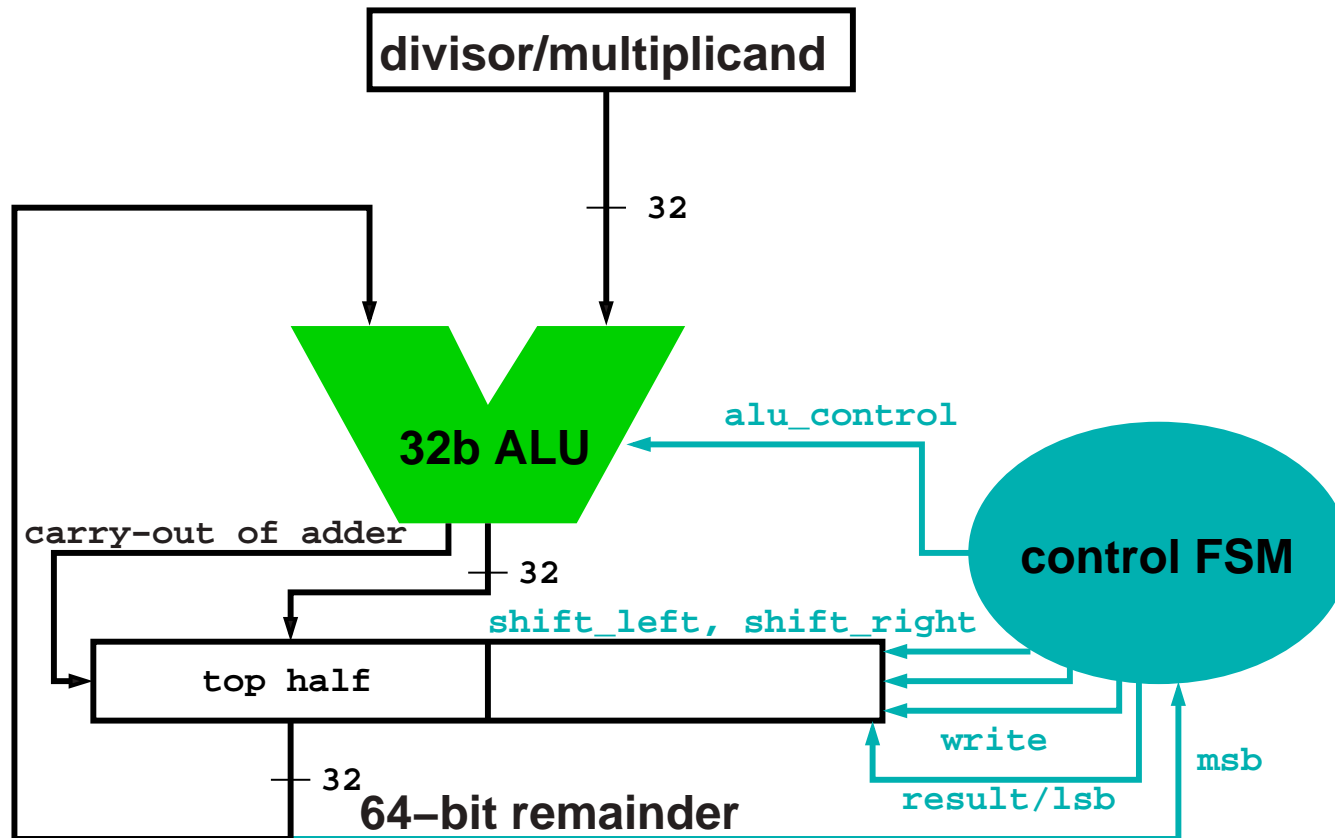

It's the same hardware...



Real Numbers

How do we represent real numbers?

Several issues:

- How many digits can we represent?
- What is the range?
- How accurate are mathematical operations?
- Consistency...

Is $a + b = b + a$?

Is $(a + b) + c = a + (b + c)$?

Is $(a + b) - b = a$?



Fixed Point

Basic idea:

0 1 0 0 1 0 1 0

radix point is here

Choose a *fixed* place in the binary number where the radix point is located.

For the example above, the number is

$$(010.01010)_2 = 2 + 2^{-2} + 2^{-4} = (2.3125)_{10}$$

How would you do mathematical operations?



Floating-Point

Some problematic numbers....

$$6.023 \times 10^{23}$$

$$6.673 \times 10^{-11}$$

$$6.62607 \times 10^{-34}$$

Scientific computations require a number of digits of precision...

But they also need *range*

⇒ permit the radix point to move

⇒ *floating-point numbers*



Floating-Point: Scientific Notation

$$\begin{array}{c} \text{sign} \\ \swarrow \downarrow \\ \pm \end{array} \underbrace{6.023}_{\text{mantissa}} \times \underbrace{10}_{\text{radix (base)}}^{\text{exponent } 23}$$

- Number represented as:
 - mantissa, exponent
- Arithmetic
 - multiplication, division: perform operation on mantissa, add/subtract exponent
 - addition, subtraction: convert operands to have the same exponent value, add/subtract mantissas

